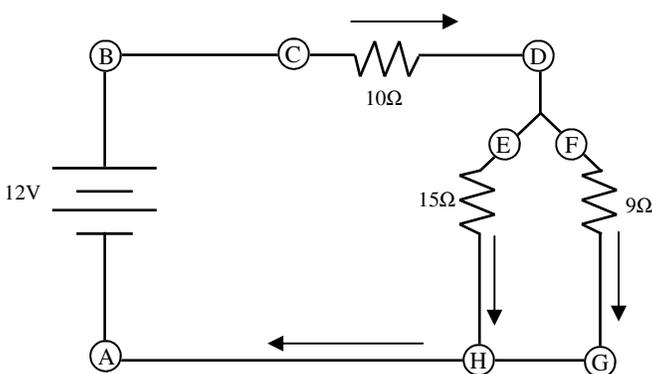


- You are given a bunch of  $20\Omega$  resistors. You can put them together in any combination of series and parallel.
  - How could you make  $100\Omega$ ?
  - How could you make a  $5\Omega$ ?
  - How could you put them together to make  $50\Omega$  worth of resistance (*get creative*)?

From the "Electrical Power" notes:

- Two light bulbs of different resistance are in series, which one is brighter?
  - Why? (*Talk about current and voltage.*)
- Two light bulbs of different resistance are in parallel, which one is brighter?
  - Why?
- \* What do these units break down?  $V =$                       Watt =                      Amp =
- \* Heat is also measure in joules. A  $3k\Omega$  resistor has  $2.5A$  flowing thru it. How much heat is does it generate in 2 minutes?
- \* A  $4.5k\Omega$  resistor is hooked up to a  $120V$  circuit. How long is it on if  $113$  coulombs passes thru it?
- Two 9-volt batteries are connected in series. If the batteries do  $36 J$  of work, how much charge is moved thru the circuit?
- \* A  $45 \Omega$  and a  $120 \Omega$  resistor are in series in a circuit. The  $120\Omega$  resistor uses  $160W$ . How much current flows thru the other resistor?

- Let me talk you thru this circuit. It would be VERY helpful if you labeled the diagram as you answer the questions. I didn't take the time to work out even numbers.






- What is the voltage at A?
- What is the voltage at C?
- \* What is the equivalent resistance for the  $15\Omega$  and  $9\Omega$  resistors?
- Redraw the simplified circuit below the original.
- From your simplified circuit what is the total resistance of the circuit?
- \* What is the total current?
- How much current is flowing thru the  $10\Omega$  resistor? (*Mark this on the original circuit.*)
- \* How much voltage is used by the  $10\Omega$  resistor?
- \* How much voltage is left at D?
- \* How much voltage is at E and F?
- \* How much current flows thru the  $15\Omega$  resistor?
- How much current flows thru the  $9\Omega$  resistor?
- If the  $15\Omega$  and  $9\Omega$  resistors were light bulbs, which one would be brighter?

10. \* Identify each of the meters at the right as an ammeter (A), ohmmeter (O), or voltmeter (V). (Put the appropriate letter in the correct circle.)

11. Which kind of meter is in parallel with a device?

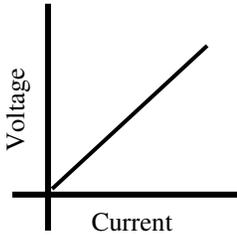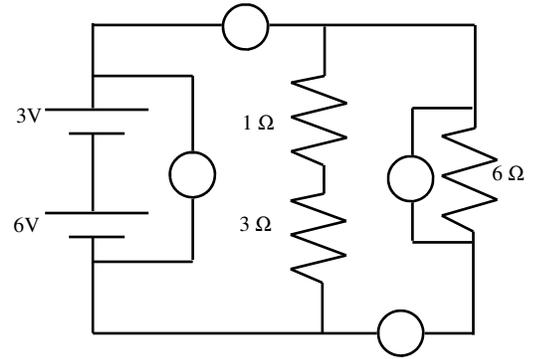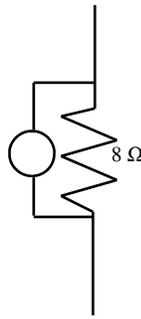12. Which kind of meter is in series with a device?



13. A. \* The slope of the line on the graph gives what?

B. How would the line change in the following situations?

- i. \* If the temperature of the conductor is lowered?
- ii. If wire is made longer?
- iii. If the wire is thicker?
- iv. If the wire is changed from silver to copper?

- Q4A:  $V = J/C$     $W = J/s$     $A = C/s$   
 Q5: 7500 W or J/s   So,  $9 \times 10^5$  J  
 Q6: 0.027 A or C/s   So, 4185 seconds  
 Q8: 1.15 A (in series, right? So same current)  
 Q9C:  $5.625 \Omega$   
 Q9F: 0.768 A  
 Q9H: 7.68 V  
 Q9I: 4.32 V (or  $12 - 4.32$ )  
 Q9J: 4.32 V (same wire)  
 Q9K: 0.288 A ( $I = V/R$ )