
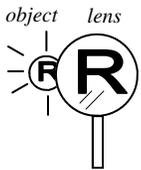


2009-10 Light 2

11. If you are using the CMYK model for making color:
- A. _____ Is CMYK paints or lights?
 - B. _____ What color is the background?
 - C. _____ How would you make Red?
 - D. _____ How would you make Cyan?
 - E. _____ What are the two ways to make black?
 - F. _____ What is the most economical way to make black?
 - G. _____ How would you make Blue?
12. If you look at a blue object thru green glasses,
- A. What color does it look like?
 - B. Why?

From the "Optics Basics" Notes:

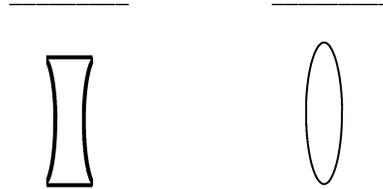13. What is the focal point?
14. Does the image come into focus at the focal point?
15. Label the two shapes at the right.



- Read about real images.*
16. You are looking thru a lens at an object.
- A. Is the image real or virtual?
 - B. Why?



And Do the TAKS Homework

Day 25—Electricity


Electricity

Electricity is the movement of electrons; Protons can't move.

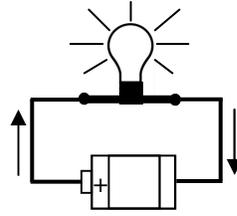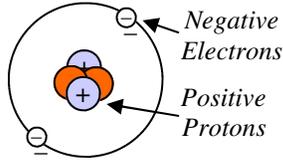Electricity flows thru conductors (like metals). Insulators resist the flow of electrons. Ionic solutions conduct electricity, too.



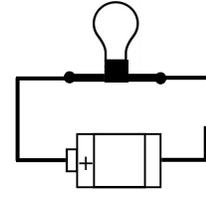A closed circuit has no break: electricity can flow.



An open circuit has a break somewhere: electricity cannot flow.

Current (in amps [A])

How many electrons flow. Like amount of water flow.

$$I = \frac{V}{R}$$

Voltage (in volts [V])

What pushes electrons. more batteries = more V = More push = more current.

Resistance (in ohms [Ω])


Like a dam holding back water. More bulbs = More R = less current.

Current equals the voltage divided by the resistance.

Types of Circuits

Series circuit—There is only 1 path for the electricity to flow. If one part of the circuit has a break (is open) the whole circuit turns off.

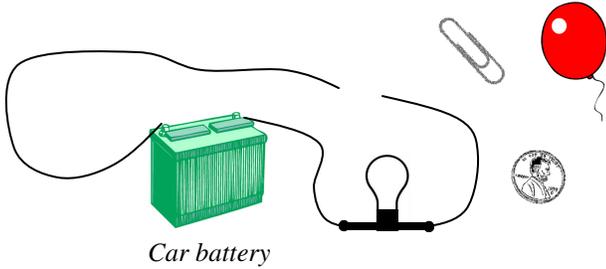
Parallel circuit—There are multiple paths for the electricity. If one part is open, the other part can stay on.




1. A. Will the light bulb light up or not (*as it is right now*)?
 - B. Why or why not?
 - C. Is it an open or closed circuit?
 - D. Which of the objects would complete the circuit?

- E. Will the light come on if you touch the two pieces of wire together?

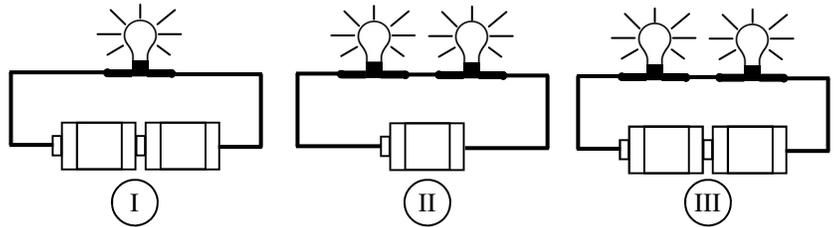2. Which circuit at the right?
 - A. Has more resistance: II or III?
 - B. Has more voltage: I or II?
 - C. Has more current: I or II?
 - D. Has more current: I or III?



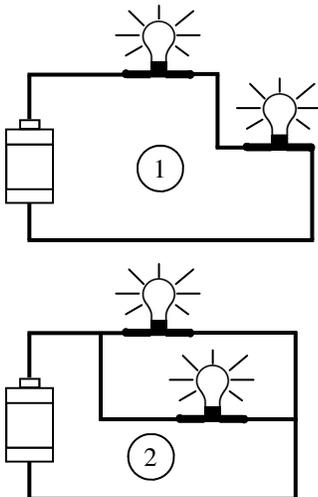3. A 9 volt battery is connected to a circuit that has a 18 ohm resistor in it. How much current flows thru the circuit?



4. Which of the two circuits at the left?
 - A. ___ Has only more than one path for the electricity to flow.
 - B. ___ Has only one path for the electricity to flow.
 - C. ___ If you disconnect one of the bulbs the other will also turn off.
 - D. ___ If you disconnect one of the bulbs the other will stay on.
 - E. ___ Is a parallel circuit.
 - F. ___ Is a series circuit.

5. A. Is your house wired in parallel or in series?
 B. How can you prove this?