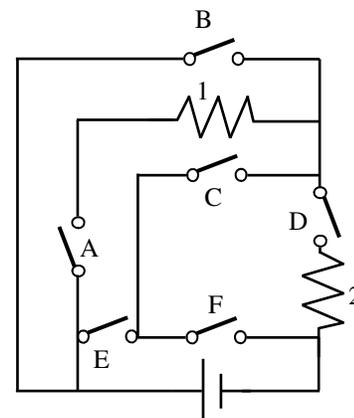


1. A. As drawn right now, is the above an open or closed circuit?
- B. With the switch is closed, what is the current in the circuit?


2. In the diagram at the right you will need to decide which switches to close to allow different situations. Start at the + side of the battery (the big side). This is like maze games—follow the path, but be sure you don't make a short-circuit.

- Which resistor or resistors allows:
- A) only resistor 1 to have current in it?
  - B) only resistor 2 to have current thru it?
  - C) to by-pass both resistors?
  - D) for electricity to go thru both resistors?



3. Work the circuit at the right and answer the following questions.

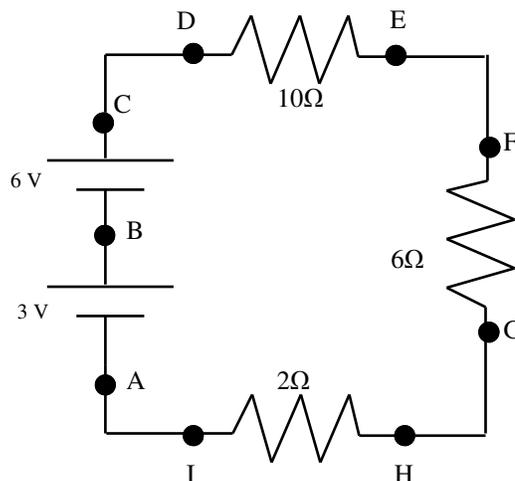- A. Calculate the current flowing thru the circuit.
- B. If one of the resistors is removed, how will the current change?
- C. If a third battery is added to the circuit, how will the current change?
- D. How much current is flowing thru the 6Ω resistor?
- E. How much voltage is used by the 6Ω resistor?
- F. How much power is used by the 6Ω resistor?
- G. Calculate how much voltage is left at point E.
- H. How much power does the whole circuit use?



Using your lab notes or the "Types of Circuits" notes:

4. Series or parallel?
 

A. ___ Only one path for the electricity to flow.	E. ___ If one light turns off, the others stay on.
B. ___ Paths are dependent on each other (one affects the other).	F. ___ If you turn off one light, all the lights turn off.
C. ___ How your house is wired.	G. ___ Has more than one path for the electricity to flow.
D. ___ Paths are independent of each other.	H. ___ Two devices have the same current.
	I. ___ Two devices have the same voltage.







5. The holes at the left are pipes.
  - A. Are the four holes in parallel or series, as shown?
  - B. Together is there a bigger hole or a smaller hole for water to flow thru?
  - C. Each pipe can allow 2 gal/sec, how much can flow thru them together?
  - D. So, is the resistance increasing or decreasing?

*This is why 4 equal resistors in parallel are the same as a single resistor that is 1/4th as big.*


6. Five 100Ω resistors are placed in a circuit.
  - A. What is the total resistance if they are in series?
  - B. What is the total resistance if they are in parallel?

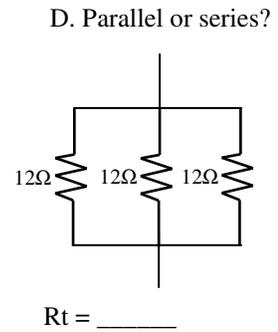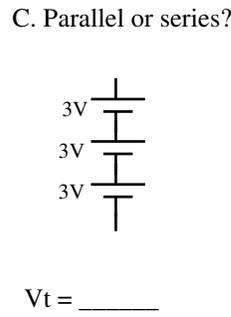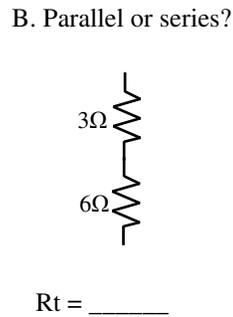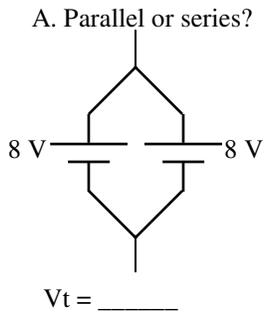7. Decide if the following are in parallel or series and find the total voltage or total resistance.



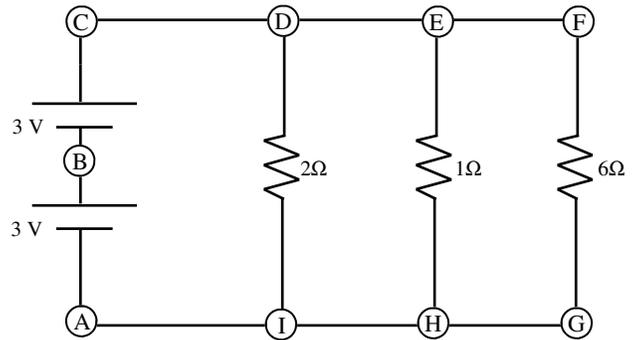
8. After working the diagram, answer the following.

- If the 6Ω resistor is disconnected, how will it affect the 2Ω resistor?
- What is the voltage at point H?
- What is the voltage at point F?
- What is the voltage from point E to point H?
- Calculate the current in each branch.
- Which resistor has the most voltage across it?
- Which resistor has the most current running thru it?
- What is the current flowing from H to I?
- What is the total current of the circuit?
- How much power is used by the 6Ω resistor?
- How much power is used by the entire circuit?



*From the Miscellaneous Circuits Lab:*

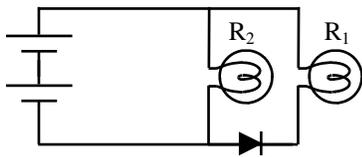9. Explain what a diode does in a circuit.



10. In the circuit at the left, R<sub>1</sub> isn't working. Without doing anything to the light bulbs, what is one change that would make R<sub>1</sub> turn on?

11. Remembering that 1 electron =  $-1.6 \times 10^{-19} \text{C}$ ... (see HW: "Electricity 1")

A. How many electrons does it take to make a charge of  $6.8 \mu\text{C}$ ?

B. What is the charge of 8.5 electrons?



	<b>Kingdom</b>	<b># of cells</b>	<b>Characteristics</b>
Prokaryotes (no nucleus)	<b>Archeabacteria</b>	unicellular (1)	Live in extreme environments (very hot, no oxygen)
	<b>Eubacteria</b>	unicellular (1)	common bacteria, live on and around us/ some are beneficial (like in our stomachs).
Eukaryotes (with a nucleus)	<b>Plants</b>	multicellular	sexual or asexual/ don't move/ cell wall of cellulose/ true roots, stems, leaves/ Autotrophs (producer own food)
	<b>Animals</b>	multicellular	move/ sexual reproduction/ heterotrophs (eats other organisms)
	<b>Fungi</b>	mostly multicellular	sexual or asexual reproduction/ cell wall of chitin/ decomposers/ Heterotrophs or saprobes (digests outside of body)
	<b>Protista</b>	multi or uni	sexual or asexual reproduction/ animal or plant-like/ auto or heterotrophs/ no cellulose or true leaves or stems

19. Which kingdom (might be more than one)?
- A. Flat worms.
  - B. Ferns.
  - C. A bacteria that lives in a thermal vent at the bottom of the ocean.
  - D. Made up of decomposers with a spongy cell wall.
  - E. Makes there own food.
  - F. Live with humans and help with digestion.