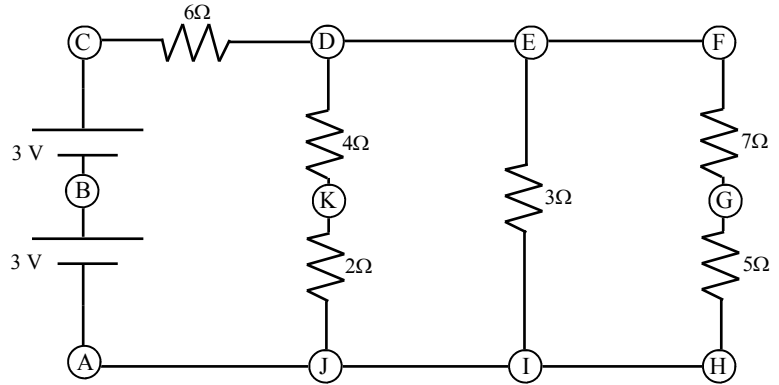


# Working a Complicated Circuit


Original circuit.

When given a complicated circuit it is always easier to simplify and redraw it. Indeed, it may take many redraws to simplify it enough to understand what's going on. Afterwards, you can work backwards to find what the current, voltage, or power in any part of the circuit.



In this redraw each of the branches is simplified with its equivalent resistance.


First redraw (simplification 1)

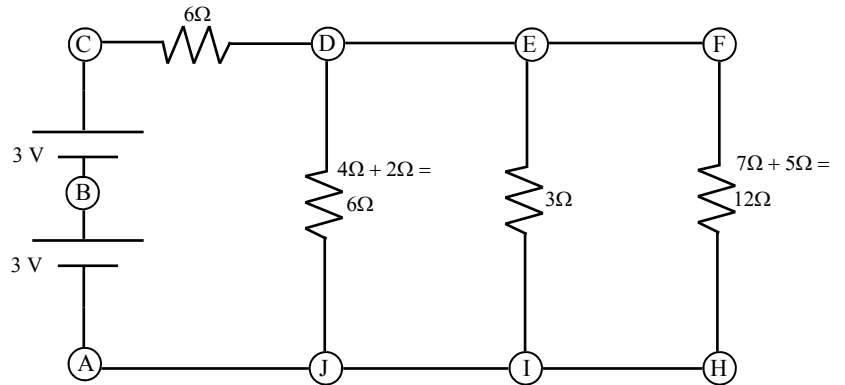

Second redraw (simplification 2)


The total resistance of the three parallel branches is found by using:
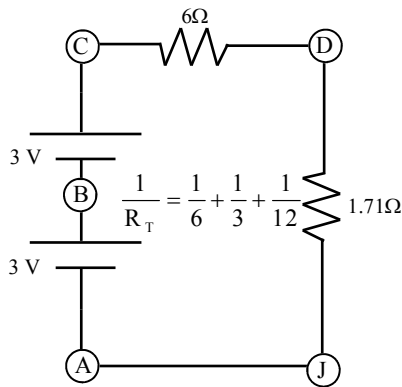
$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$



Third redraw (simplification 3)

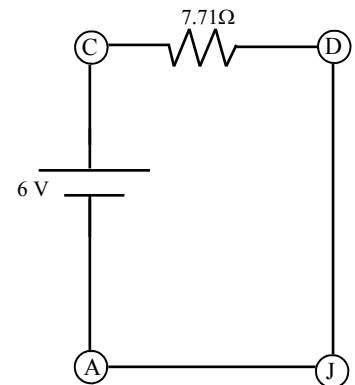
Since the 6Ω and 1.71Ω are in series, we just add them together find the total resistance of the circuit.




Now that you have the total resistance (7.71Ω) you can find the total current and start working backwards, as I will do on the second page.

Instead of showing the work on the previous page, this page shows exactly how to work backwards thru the circuit.

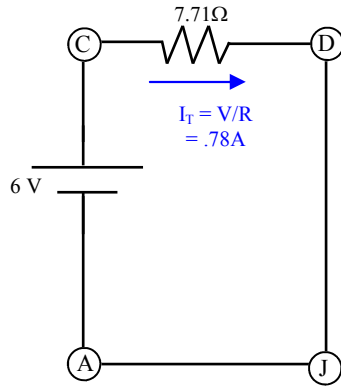
Third redraw  
(simplification 3):  
Find total current  
from total voltage  
and resistance.



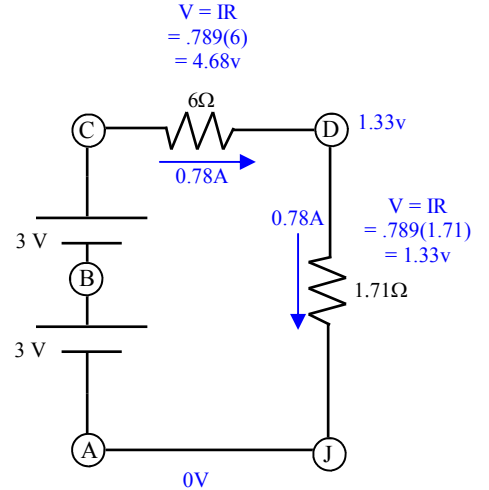Second redraw  
(simplification 2):  
Find the voltage  
from D to J.



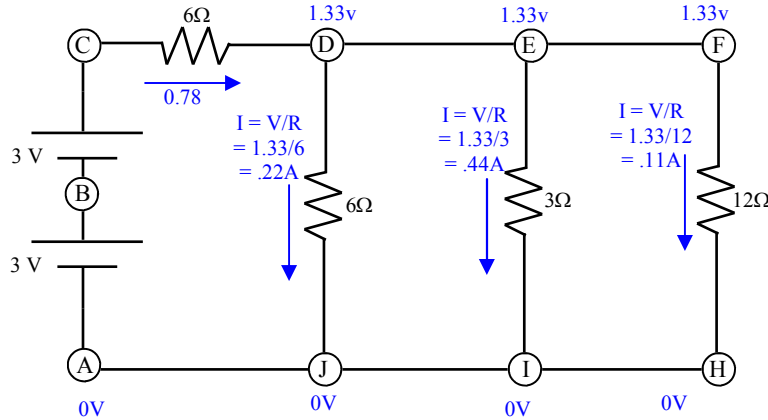First redraw  
(simplification 1):  
Now that you know the  
voltage from D to J,  
you can find the cur-  
rent in each branch.



Original circuit.  
Now that you  
have the current in  
each branch, you  
know the current  
in each resistor  
and can calculate  
any necessary  
quantity.

