

## 2008 Electricity 5

Equations	
In Series	$R_T = R_1 + R_2 + \dots$
In Parallel	$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$

Example: 3 resistors are in parallel:  $4\Omega$ ,  $5\Omega$ , and  $7\Omega$ . Find the total resistance of three resistors.

Solution: Since in parallel use:

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

$$\frac{1}{R_T} = \frac{1}{4} + \frac{1}{5} + \frac{1}{7}$$

$$\frac{1}{R_T} = .25 + .2 + .143$$

$$\frac{1}{R_T} = .593$$


$$R_T = \frac{1}{.593} = 1.7\Omega$$

1. Series or parallel?

- |  |  |
|--|--|
| A. ___ Only one path for the electricity to flow.                    | E. ___ If one light turns off, the others stay on.         |
| B. ___ Paths are dependent on each other<br>(one affects the other). | F. ___ If you turn off one light, all the lights turn off. |
| C. ___ How your house is wired.                                      | G. ___ Has more than one path for the electricity to flow. |
| D. ___ Paths are independent of each other.                          | H. ___ Two devices have the same current.                  |
|  | I. ___ Two devices have the same voltage.                  |


2. Decide if the following are in parallel or series and find the total voltage or total resistance.

A. Parallel or series?

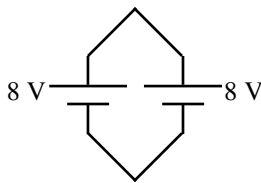


$V_t = \underline{\hspace{2cm}}$

B. Parallel or series?

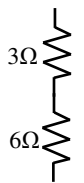


$V_t = \underline{\hspace{2cm}}$

C. Parallel or series?

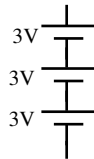


$V_t = \underline{\hspace{2cm}}$

D. Parallel or series?

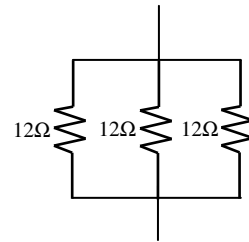


$V_t = \underline{\hspace{2cm}}$

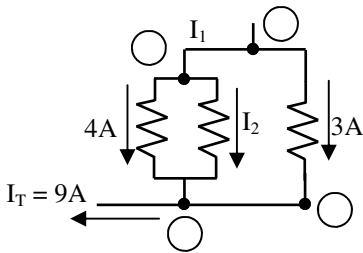


3. A. In each of the circles at the left, label them as S (split) or J (join).  
 B. Use the diagram, what is  $I_1 =$   
 C.  $I_2 =$

4. What do we call a place where electricity splits in a circuit?

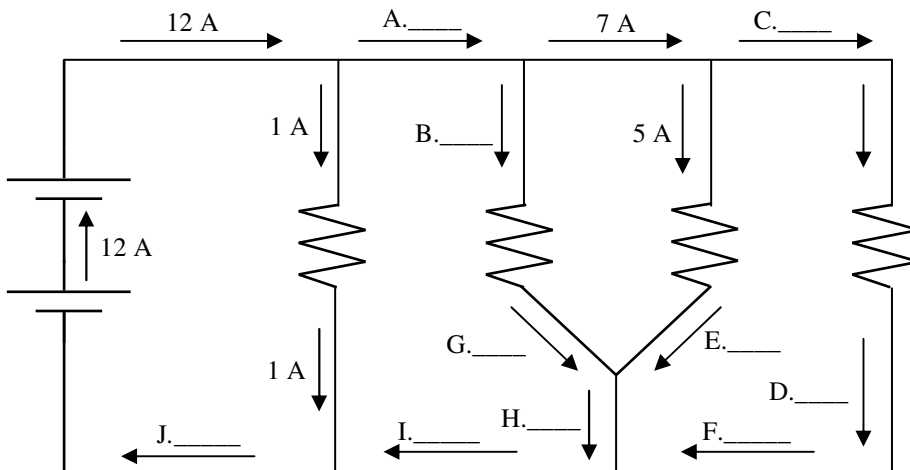
5. Objects in series have the same \_\_\_\_\_. Objects in parallel have the same \_\_\_\_\_.



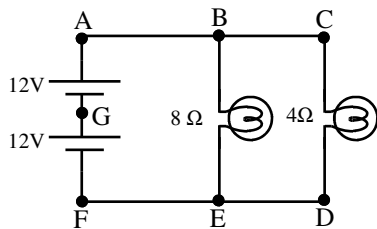6. A. Fill in the blanks in the diagram.  
 Big Hint: Fill them in in order.  
 B. What is the total current in the circuit?  
 C. If each battery is 3 v, what is the total voltage?  
 D. What is the total resistance of the circuit?



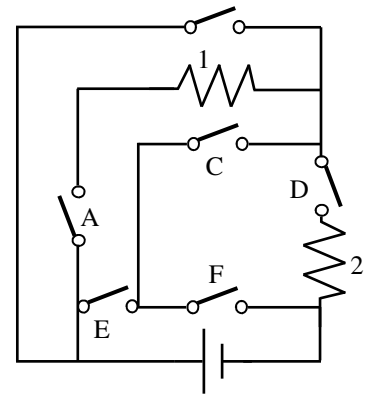7. Use the diagram to answer:
- A) Total voltage:
  - B) Parallel or series?
  - C) Which light bulb will have more current flowing thru it?
  - D) V at F?
  - E) V at B =
  - F) V from B to E ( $V_{BE}$ ) =
  - G) Find the current going thru the  $8 \Omega$  resistor.
  - H) Find the current going thru the  $4 \Omega$  resistor.
  - I) What is the  $I_T$ ?



8. In the above diagram, which switches allow:
- A) only resistor 1 to have current in it?
  - B) only resistor 2 to have current thru it?
  - C) to by-pass both resistors?
  - D) for electricity to go thru both resistors?

9. From your book: If current is the amount of charge that flows each second (Amps = Coulombs/Sec), then how many electrons flow in 4 seconds from a 1.5 amp circuit?