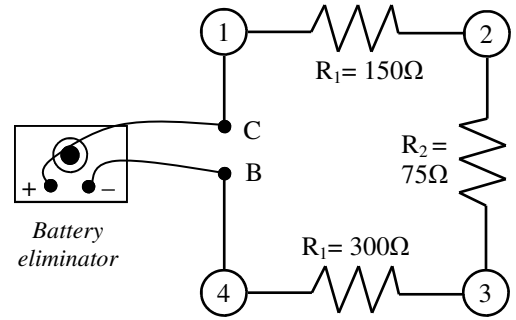


2008 PreAP Circuits 3

1. The circuit at the right has four ammeters in it to measure the current at each corner.
 - A. If the battery eliminator is on, is the circuit open or closed?
 - B. What happens if you put a wire between C and B?
 - C. What is the total resistance of the circuit?



- D. If the battery eliminator is set to 9v, find the current in the circuit.

- E. What do the different ammeters read?

$I_1 = \text{_____}, I_2 = \text{_____}, I_3 = \text{_____}, I_4 = \text{_____} .$

- F. How much current is flowing thru the R1?
- G. How much voltage does R₁ use?


- H. Calculate the voltage used by each resistor.

- I. Since $V = IR$ and $P = VI$,
 - i. Derive an equations for power that does not include voltage.

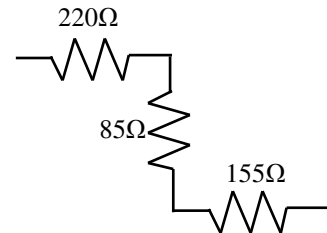
- ii. Derive an equation for power that does not include current.

- J. If each of the resistors is a light bulb, which one is the brightest?

- K. Then the 75Ω resistor is replaced by a wire.
 - i. Which ammeter changes?
 - ii. What does each ammeter read ?



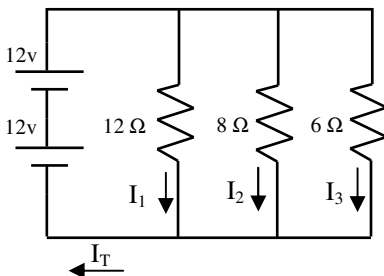2. What is the total resistance of the three resistors shown at the right?




3. A. Calculate the total resistance of the three resistors in the circuit at the left.

- B. Calculate V_{total} .


- C. What is the difference of voltage across each of the three resistors?

- D. Calculate (and label) $I_1, I_2,$ and I_3 .

- E. What is the total current?

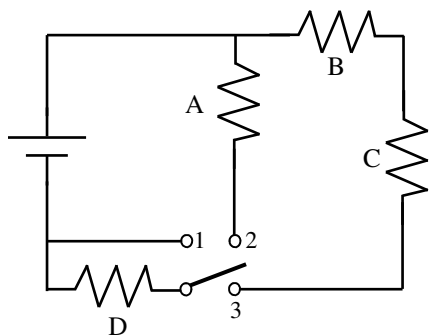

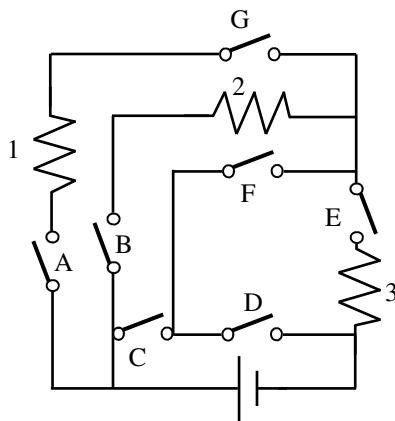4. A. In order for resistor A to light, the switch must be at position: ____.
- B. Are resistor A and B in series or parallel?
- C. If the switch is at position 3, B, C, and D are in series or parallel?



5. A. To make only resistor 1 on:
- B. To make only resistor 3 on:
- C. To make only resistor 1 and 3 on:

Work these problems from the book:

Starting on page 717:

Q10, 11, 14, 16, 17, 18, 21, 23, 34.

And on page 755: Q 16, 17, 18, 19