

## 2008 PreAP Circuits 4

1. Using  $V = IR$  and  $P = VI$ , find the resistance of a 40W light bulb when connected to 120 V power supply.


2. Use the following circuit to answer the following questions.

A. Calculate the equivalent resistance of the circuit. HINTS: If resistors are in series, reduce

them to one resistor using  $R_T = R_1 + R_2 \dots$ . If resistors are in parallel use:

You will have to do this multiple times. Redrawing will be essential.
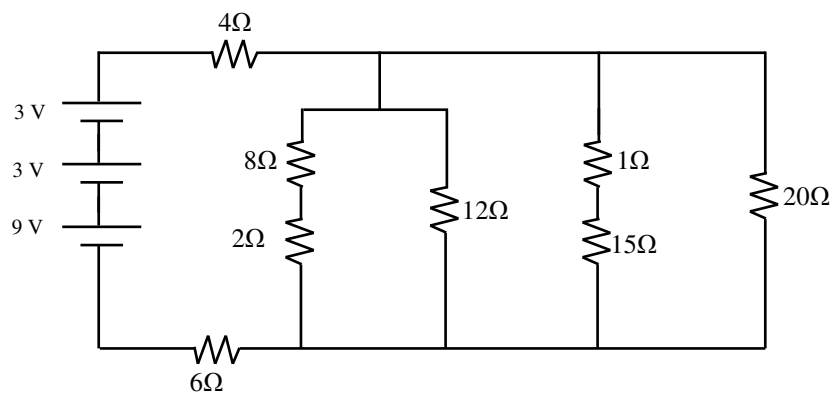
$$\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots$$



- B. Determine how much current is flowing thru the 8Ω resistor.  
HINT: Work backwards.