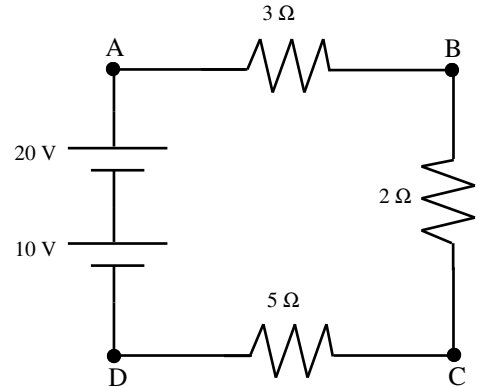


2008 PreAP Circuits 5


1. After working the circuit at the right, answer the following questions.

- A) $I_{\text{thru } 2\Omega} =$
- B) $I_{\text{thru batteries}} =$
- C) $V_{\text{used by } 5\Omega} =$
- D) $P_{\text{used by } 3\Omega} =$
- E) $V_{\text{at C}} =$
- F) $P_{\text{total}} =$
- G) If the 5Ω resistor is increased to a 10Ω resistor, what happens to the current?
- H) Which resistor uses the most voltage?
- I) Which resistor uses the most power?
- J) If they were light bulbs, which one would be the dimmest?
- K) In what situation could there be $0A$ flowing thru point D?
- L) The second battery is then replaced by a $9v$ battery (so that there is less total voltage). Which resistor would have the most current flowing thru it?




2. After working the circuit at the right, answer the following questions.

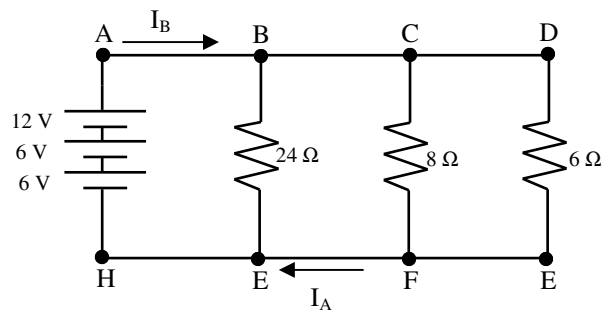- A) $I_{\text{thru } 6\Omega} =$
- B) $I_{\text{thru batteries}} =$
- C) $V_{\text{used by } 24\Omega} =$
- D) $P_{\text{used by } 8\Omega} =$
- E) $V_{\text{at C}} =$
- F) $I_A =$
- G) $I_B =$
- H) $P_{\text{total}} =$
- I) Which resistor uses the most voltage?
- J) Which resistor allows the most current?
- K) Which resistor uses the most power?
- L) If they were light bulbs, which one would be the brightest?
- M) The 6Ω is then replaced by a 12Ω resistor.
 - i) The current flowing thru the 12Ω would increase or decrease?
 - ii) The current flowing thru the 8Ω would increase or decrease?
 - iii) The total current provided by the batteries would increase or decrease?
 - iv) The voltage used by the new 12Ω would increase or decrease?



3. Answer the following questions about the circuit below.

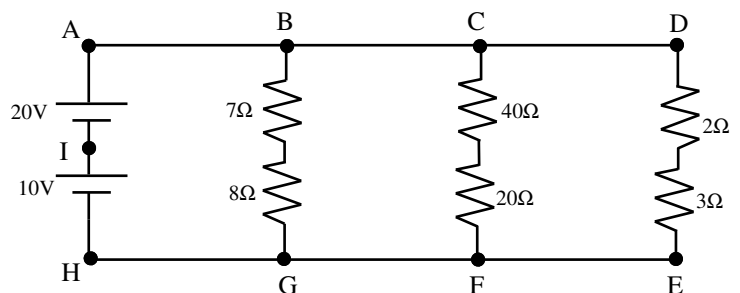- A) The 40Ω and 20Ω are in parallel or series which each other?
- B) $I_{\text{from F to G}} =$
- C) $I_{\text{Total}} =$
- D) $I_{\text{from C to D}} =$
- E) $V_{\text{from B to D}} =$
- F) $V_{\text{at F}} =$
- G) $V_{\text{used by the } 2\Omega} =$
- H) $P_{\text{used by the } 8\Omega} =$
- I) If the 20Ω resistor is changed to 10Ω ,
 - i) how does the current from B to G change?
 - ii) how does the total current change?
- J) How much energy does the 8Ω resistor use in 20 seconds?
- K) What are the units for heat?
- L) How much energy does the 8Ω resistor dissipate in 20 seconds?



4. If your electric company were to sell electricity at a cost of 8 cents per kilowatt hour, how much would it cost to run a 400 W appliance for 3 hours?

5. Why is it that metals are good conductors. Also talk about them on an atomic or at least molecular level.

6. Using the electrical symbols, draw a diagram with two light bulbs, two batteries and a switch so that each of the light bulbs can be turned off independently.

7. In a circuit the words “potential difference” refers to what quantity?

8. Using the circuit at the right answer the following questions.

- A) Calculate the total equivalent resistance.

- B) Calculate the EMF of the battery.

- C) Calculate the power dissipated by the 12Ω resistor.

- D) If the three resistors were light bulbs, which one would be brightest?
(You must justify your answer.)

- E) How many electrons travel thru R_1 in 10 seconds?

