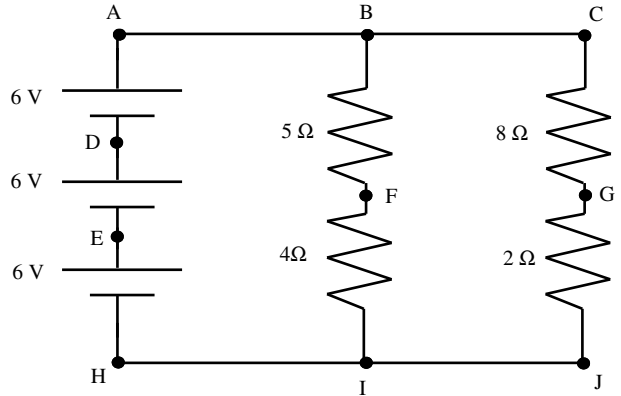


2009 PreAP Circuits 3

- What is the voltage at point B?
 - What is the total resistance from B to I?
 - What is the current from B to I?
 - What is the current from C to J?
 - What is the total current?
 - What is the current flowing thru the 5Ω resistor?
 - What is the voltage used by the 5Ω resistor?
 - What is the power used by the 8Ω resistor?
 - How much **energy** is used by 4Ω resistor in 20 seconds?
 - How would the current change in the 5Ω resistor if the 4Ω resistor was increased?
 - How would the current in the 2Ω resistor change if the 4Ω resistor was removed?





- A 25Ω resistor at 5°C or at 25°C ?
 - A 5 cm wire or a 5 meter wire?
 - Thick wires or thin wires?
 - Aluminum wires or Copper wires?

3. Is a superconductor a good or bad insulator?

4. AC or DC Current:

- | | |
|---------------------------------------|--|
| A. ___ Current that changes polarity. | D. ___ What comes from the power outlet. |
| B. ___ Current that is constant. | E. ___ Graph A |
| C. ___ What comes from a battery. | F. ___ Graph B. |

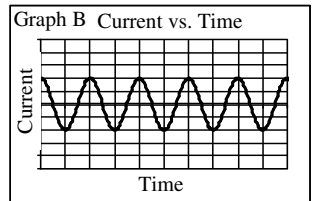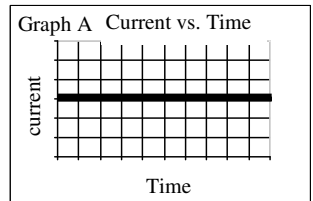

- How much voltage is used by the 6Ω resistor?
 - How big is the second resistor?
 - How much energy is used by the 10Ω resistor in 2 minutes?
 - What would happen to current in the 10Ω if the 6Ω is increased?
 - If the voltage is increased, how does the power dissipated in the middle resistor change?
 - Draw a voltmeter reading the total voltage.

