

## 2008 Electricity 10 (Test Review)

1. Draw the electric field lines that will occur between the two charges.




2. A. Identify the meters in Circuit A:  
 M1: \_\_\_\_; M2: \_\_\_\_; M3: \_\_\_\_; M4: \_\_\_\_.

B. What does meter 1 read?

C. What is the voltage at B?

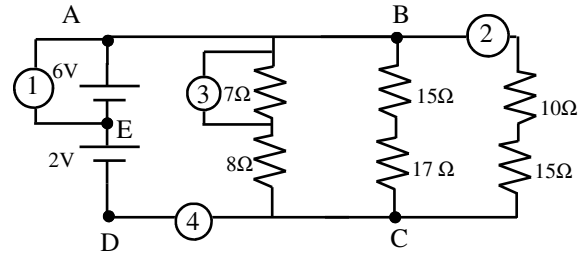3. A. Find the electric field 2 cm away from a  $8\mu\text{C}$  charge.




B. Because the equation has an  $r^2$  in the denominator (bottom), if the charge is moved to 4 cm away, by how much does the electric field's strength change?

4. Decide which switches in Circuit B need to close to allow the following:

- A. Only resistor A on:
- B. Only resistors A and B on:
- C. Only resistors A and C on:
- D. Only resistors A, B, and D on:

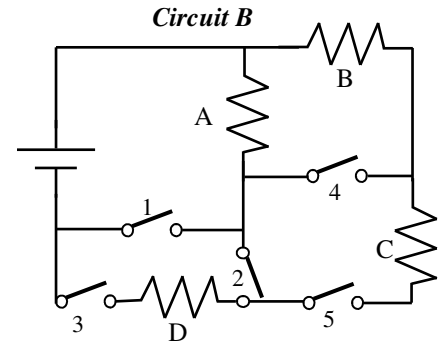
5. A. Find the force between a 6 C and a  $-3\text{C}$  charge if they are 4 meters apart.



B. Is this force attractive or repulsive?


- 6. A. If a balloon rubbed with fur becomes negative, did it gain or lose electrons?
- B. If a negative object touches ground, what happens?

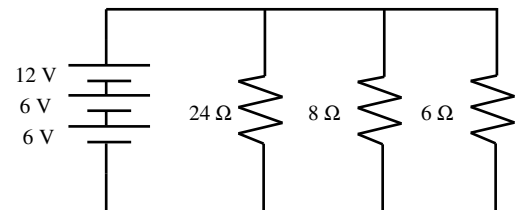7. A) In Circuit C, which light bulb is brighter?  
 B) Why? (*Be specific.*)



8. A) Is your house in series or parallel?  
 B) How do you know for sure?

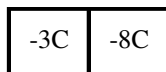9. How can you prove that a circuit is in series?




- 10. A) Will two electrons attract or repel each other?
- B) If two electrons are brought closer together, will the force between them increase or decrease?
- C) If even more electrons are brought close to each other, will the force between them increase or decrease?
- D) Of the two square objects at the right, which object has more electrons?
- E) Since the two objects are the same size, which side's electrons are experiencing a greater force of repulsion?
- F) So, which direction will the electrons move?

11. A. Find the current in the circuit.

B. How much voltage is used by the  $10\Omega$  resistor?

C. How much voltage is left at the upper right hand corner?

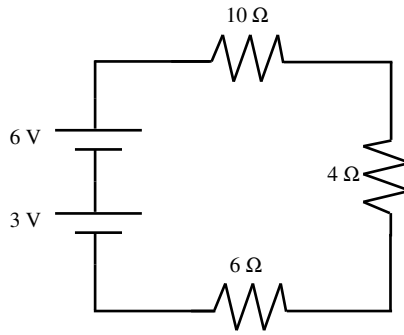D. How much power is used up in the entire circuit?



12. Make sure you know these terms:

- |                    |                   |                             |
|--------------------|-------------------|-----------------------------|
| A. Capacitor       | F. Insulator      | K. Electric Force           |
| B. Fuse            | G. Conductor      | L. AC (alternating current) |
| C. Circuit breaker | H. Parallel       | M. DC (Direct current)      |
| D. Short circuit   | I. Series         |                             |
| E. Superconductor  | J. Electric Field |                             |

13. Study what factors affects resistance.

14. A. Know what all of these are: resistors; battery; wire; light bulb; switch.

B. Know how to draw them.

15. On the diagram below, Object B has been made negative by rubbing it with fur.

A. In the first picture (left) draw where the negatives are on Object A.

B. If you touch object A while it is touching to object B, where will the negatives go?

C. After you touched Object A, (bottom picture) will it have a positive or a negative charge?

D. This is called charging by: \_\_\_\_\_.

