

A-day: Due Tues., Apr 15 (Assigned Tues., Apr 10) B-day: Due Wed., Apr 16(Assigned Wed., Apr 11)

2008 Electricity 6

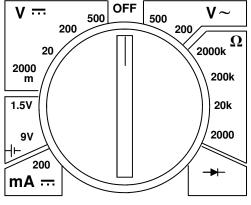


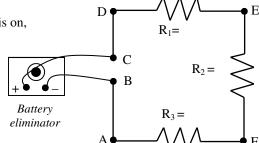


- Use the multimeter at the left to answer the following questions.
 - A. Circle the setting we used for measuring resistance.
 - B. Put a square around the setting we used to measure voltage.
 - C. If you are trying to measure resistance and the meter says ", what does it mean?
 - D. What does the "k" signify?
- What did the blue metal boxes substitute for?
- In the diagram at the right, notice the gap between points C and D.
 - A. If the battery eliminator is on, is the circuit open or closed?
 - B. What happens if you put a wire between C and D?




- Ohmmeter, Voltmeter, or Ammeter?
 - Must be in series.
 - B. _____The circuit cannot connected.
 - C. _____Must be in parallel with the device being measured.
 - __What is being measured in the circuit at the right.
 - ____The circuit must be on.
 - F. __Delicate. Can be damaged if hooked up wrong.
 - ____Can tell you if a battery is worn out. G.
 - H. __Can measure a resistor only in a circuit.
 - I. __Can measure a resistor out of the circuit.
- What is the total resistance of the three resistors shown at the right?

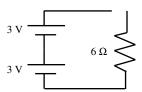

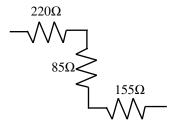


- 12 Ω 8Ω
- A. Calculate the total resistance of the three resistors in the circuit at the left.
 - B. Calculate V_{total}.
 - What is the difference of voltage across each of the three resistors?
 - Calculate (and label) I_1 , I_2 , and I_3 .
 - What is the total current?

2008 Electricity 6

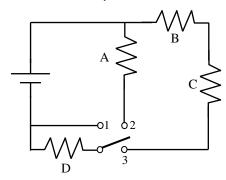

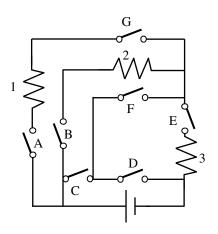- A. In order for resistor A to light, the switch must be at position:
 - B. Are resistor A and B in series or parallel?
 - C. If the switch is at position 3, B, C, and D are in series or parallel?



- 8. A. To make only resistor 1 on:
 - B. To make only resistor 3 on:
 - C. To make only resistor 1 and 3 on:

Seniors may stop.

- Bacteria or Virus?
 - A. ____ Is alive.
 - B. ____ Has no nucleus.
 - C. ____ Causes AIDS.
 - D. ____ Has only parts of DNA, but not complete.
- 10. Photosynthesis or Respiration?

 - B. ____Uses glucose.

 - D. ____Uses energy.

- E. ____Can cause diseases.
- F. ____Can be helpful.
- G. ____Can be killed by antibiotics.
- H. ____Does not have organelles.
- E. ___ Makes energy. A. Produces carbon dioxide.
 - F. ___ Produces water.
- C. ____Makes glucose. G. ___ Done by plants.
 - H. ___ Done only by plants.
- 11. Which body system?
 - A. Keeps the species from going extinct.
 - B. Uses electricity to send information to the body from the brain.
 - C. Includes small and large intestines.
 - D. Removes excess water and unwanted wastes from the body.
 - E. Uses chemicals to remove the nutrients of food to be used by the body.
 - F. Keeps contaminants from entering the body and moisture from escaping.
 - G. Moves the bones AND helps move blood around the body, helping the heart.
 - H. Gets oxygen and food to the individual body systems and cells.
 - I. Include veins and arteries.
 - J. Uses white blood cells to fight diseases.
 - K. Protects your brain and allows us to keep our shape.
 - L. Moves oxygen into and CO_2 out of the body.
 - M. Gives off chemicals to make the body "want to do things", including fight, run, cry, be afraid, etc.
 - N. The centers of this system makes blood for the circulatory system.
 - O. Made up of interconnected neurons.