
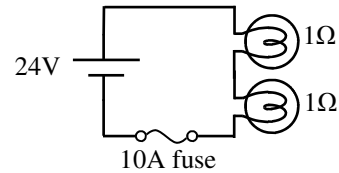


- From "Meters" notes:  
 A. Each of the four circles in the circuit at the left are meters. In each of the circles put one of the following: Ammeter (A); Ohmmeter (O); Voltmeter (V).
- What is the total current in the circuit at the left?
- Since  $1 e = -1.6 \times 10^{-19} C$ , how much charge does 5.4 electrons have?



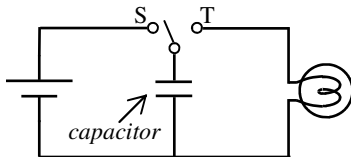
- Use the circuit at the right to answer the following. (Notes: "Power and Voltage Drops").  
 A. What is the current flowing in the circuit?  
 B. What will happen to the fuse?



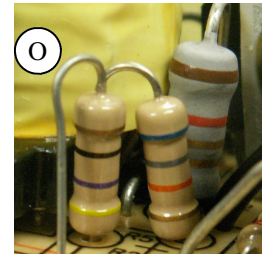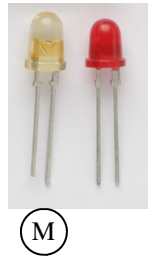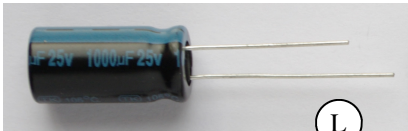
- A. Can you reset a fuse?  
 B. Can you reset a circuit breaker?



- The circuit at the left shows a capacitor like the red plastic one you used in the circuit boards. The switch can be switched between point S and point T. The switch is first put to point S. Then the switch is moved to point T. Describe what happens.





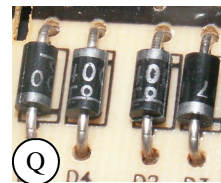
- Identify the pictures above:  
 A. \_\_\_ Resistor.  
 B. \_\_\_ Diode  
 C. \_\_\_ Fuse  
 D. \_\_\_ Capacitor  
 E. \_\_\_ Variable resistor  
 F. \_\_\_ Light emitting diode.  
 G. \_\_\_ Can protect a circuit from too much current.  
 H. \_\_\_ Only lets the current flow one way.  
 I. \_\_\_ Stores charge temporarily.  
 J. \_\_\_ Used by an oven to change temperature.



- What are the colored strips for on a resistor?

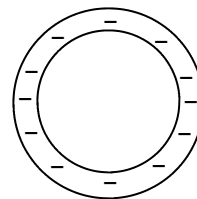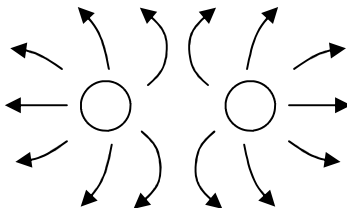- From the Electric field notes OR the Electric field game (link on website):  
 A. Identify the charges below.  
 B. Draw the electric field of the ring below (inside and out).



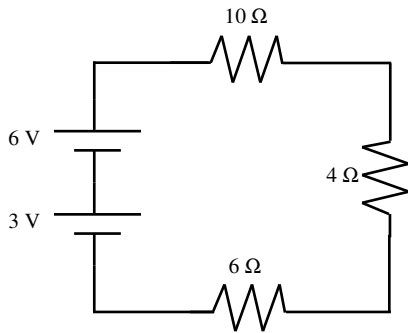


10. Use the circuit at the left to answer the following.
- What is the total current?
  - How much voltage is used by the 4Ω resistor?


- How much power is used by the 6Ω resistor?

The 10Ω resistor is then replaced by a wire.

- How does the current in the 6Ω change?

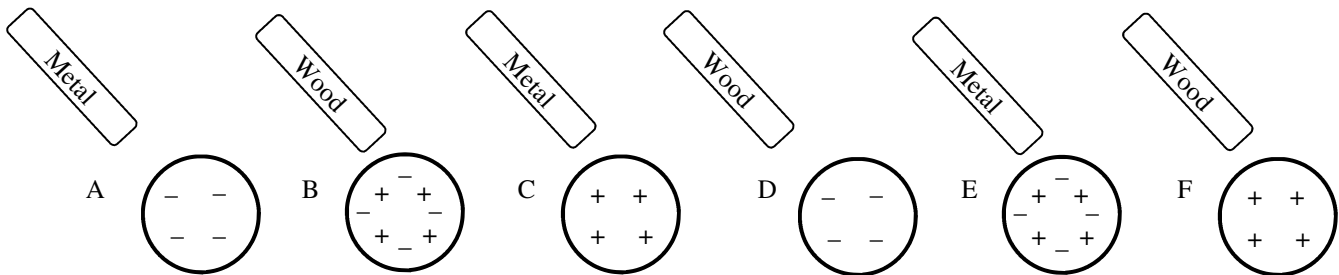

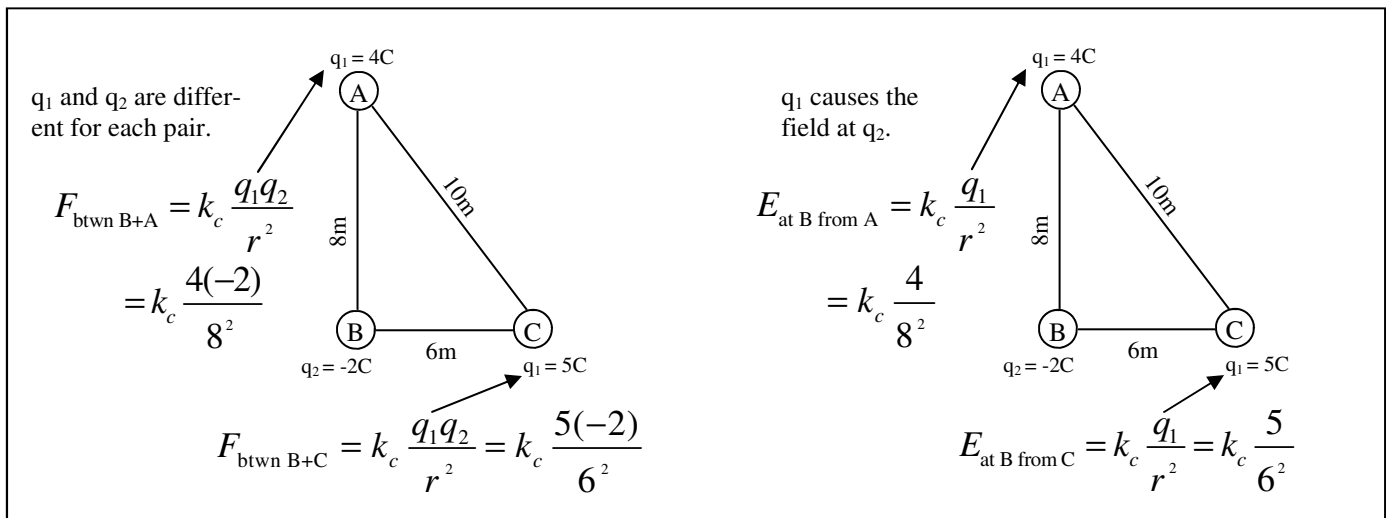11. The long objects above depict metal or wooden rods. The circular objects show positive, negative, or neutral objects.
- What moves: electrons or protons?
  - On which object will charges be able to flow: the metal or wood object above?
  - For each example above, show electrons moving away or toward the object. If no electrons move, leave the bar alone.



12. After studying the diagrams above, answer the following questions:
- If you were trying to find the electric field from A at C,
    - What is  $q_1$ ?
    - What is  $q_2$ ?
    - How would E change if charge C were decreased?
  - Calculate the electric field at A due to C.
  - Calculate the force between A and C.