

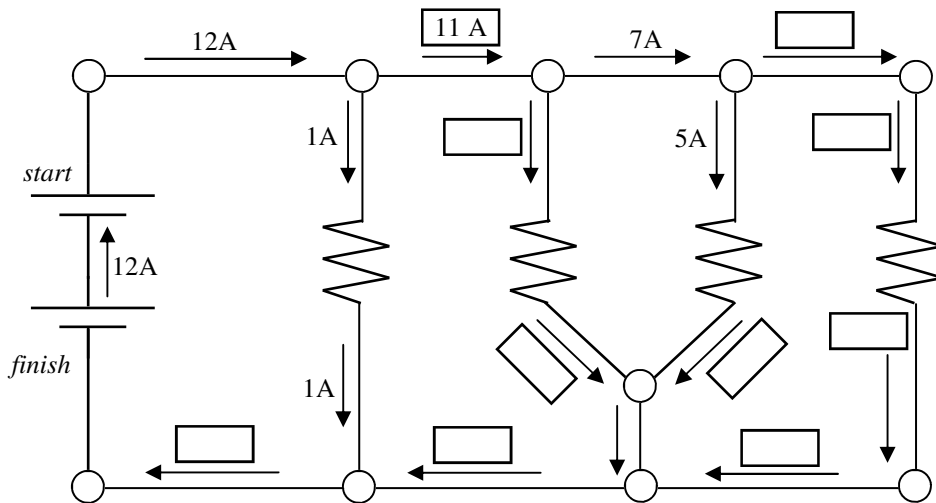


2009 Electricity 7

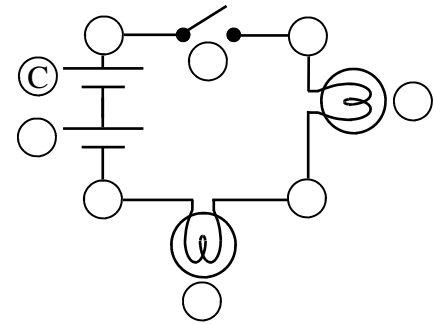

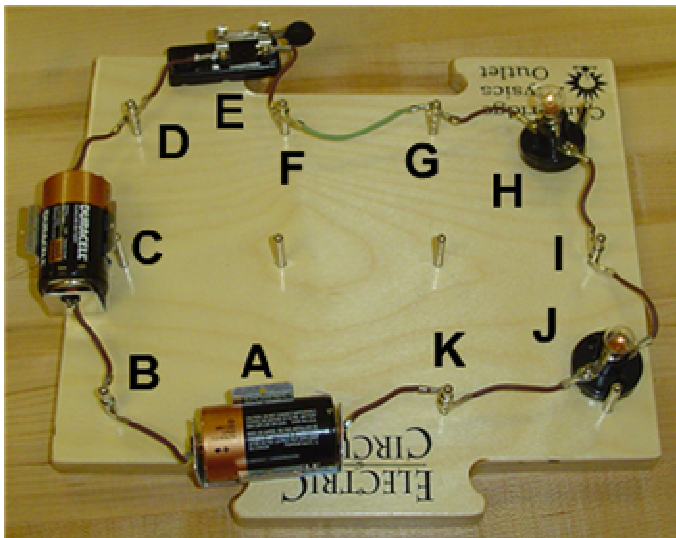
- The circuit at the right will help you understand current. Start at the top of the batteries (at "start").
 - In each of the circles, put one of the following:
 S (split) - one wire splits into 2.
 J (join) - two wire combine
 T (turn) - wire only turns.
 - In each of the boxes, fill in the current for that part of the circuit. (*Hint: this is just addition and subtraction.*)





- For each of the circles on the circuit diagram above, put the corresponding letter from the picture at the left. One of them is already done for you.

- After working the circuit at the right, answer the following questions.

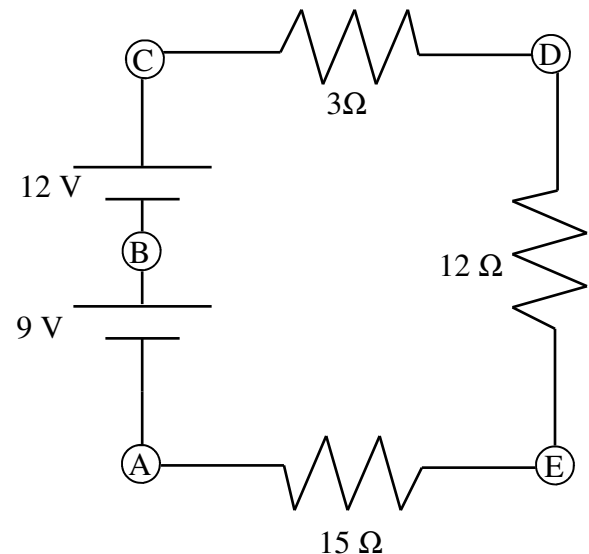
- Just by looking, which resistor uses the least amount of voltage?
- What is the total current?
- How much voltage is used by the 12Ω resistor?
- How much power is used by the 15Ω resistor?
- What is the voltage difference between point C and point E?
- What would happen if you increased the 12Ω resistor?
- What is the current if the 15Ω resistor is short-circuited?



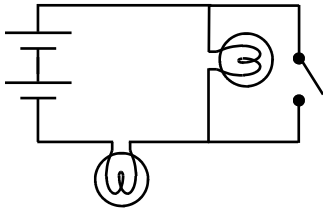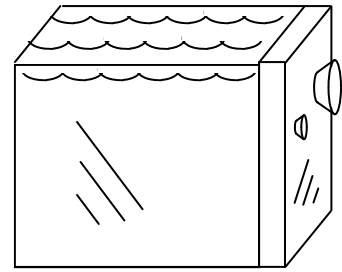
4. Imagine a large tank of water. In one side of the tank are two holes with plugs in them: a large hole and a small hole.
- When removed, which hole will have more resistance?
 - Which hole will have more water flow through it?
 - Water, like electricity, always takes the path of:



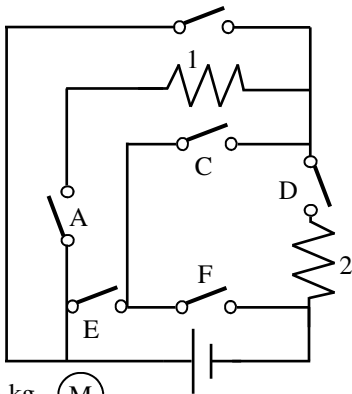
5. From the Lab (see the diagram at the left) -
- When the switch is open (as shown), which path is less resistance: the light bulb or the switch?
 - When the switch is closed, which path is less resistance: the light bulb or the switch?
 - When the switch is closed, will bulb 1 get brighter or dimmer?
 - Why?
 - What happens if you put a wire across the terminals of a battery (between the positive and negative ends of a battery)?
 - How could this be dangerous?



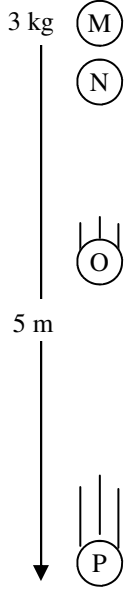6. In the diagram at the left you will need to decide which switches to close to allow different situations. Start at the + side of the battery (the big side). Which resistor or resistors allows:
- only resistor 1 to have current in it?
 - only resistor 2 to have current through it?
 - to by-pass both resistors?
 - for electricity to go through both resistors?



7. (From the “Meters” notes) Identify the meters in the diagram at the right.
- | | |
|-------------|-------------|
| A. Meter 1: | B. Meter 2: |
| C. Meter 3: | D. Meter 4: |
| E. Meter 5: | |

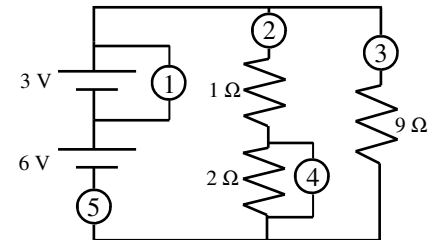

8. A ball is dropped from 5 m in the air. It is at rest to begin with.
- Calculate its initial energy.
 - How much work was done on the ball to lift it to its initial point?
 - What kind of energy is it losing as it falls?
 - What kind of energy is it gaining as it falls?
 - What is the initial speed of the ball?
 - What is the weight of the ball?
 - What is the acceleration of the ball as it falls?
 - Each second, does the amount of distance it falls increase, decrease or remain constant?
 - What is the displacement of the object (what is its vertical change of position)?
 - How fast is it going just before it hits the ground? (*You can do this two ways.*)

9. A ball is rolling thru a tube, as shown. Just as the ball is exiting the tube,
- Toward which point does the object’s velocity point?
 - Toward which point does the force on the object point?
 - Toward which point does the object’s acceleration point?
 - Toward which point does the ball move after it leaves the tube?
 - What do we call the force that moves an object around a circle?
 - What provides this circular force in this case?

