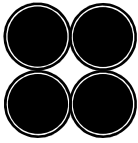






**NOTE: For B-day this homework is due the Friday AFTER TAKS. Your TAKS homework is due before TAKS.**



1. The holes at the left are pipes.
  - A. Are the four holes in parallel or series, as shown?
  - B. Together is there a bigger hole or a smaller hole for water to flow thru?
  - C. Each pipe can allow 2 gal/sec, how much can flow thru them together?
  - D. So, is the resistance increasing or decreasing?


*This is why 4 equal resistors in parallel are the same as a single resistor that is 1/4th as big.*

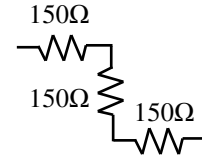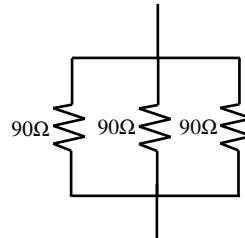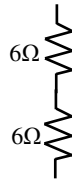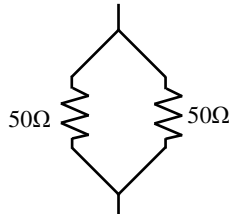2. For each of the following examples decide if they are in parallel or series and calculate the total resistance.




- |  |  |  |  |
|--|--|--|--|
| A. Parallel or series?<br>$R_{total} = \underline{\hspace{2cm}}$ | B. Parallel or series?<br>$R_{total} = \underline{\hspace{2cm}}$ | C. Parallel or series?<br>$R_{total} = \underline{\hspace{2cm}}$ | D. Parallel or series?<br>$R_{total} = \underline{\hspace{2cm}}$ |
|--|--|--|--|


*From the Lab:*

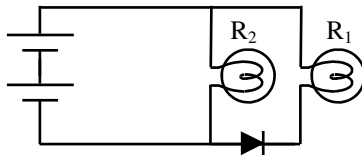

3. Explain what a diode does in a circuit.
4. In the circuit at the left,  $R_1$  isn't working. Without doing anything to the light bulbs, what is one change that would make  $R_1$  turn on?

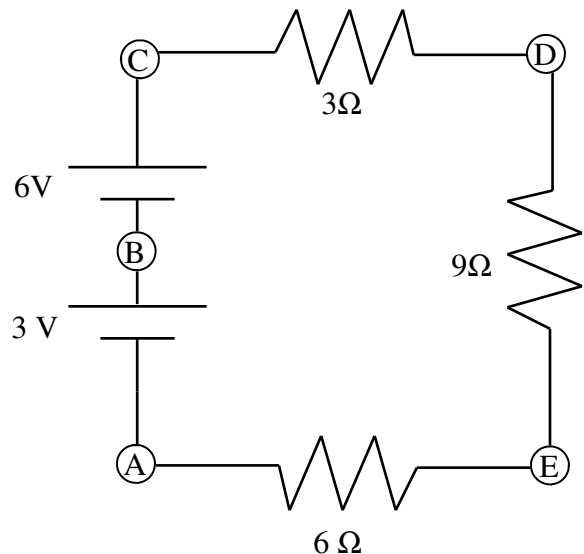5. Given these two light bulbs:  $5\Omega$  and  $8\Omega$ .
  - A. When in series, which light bulb is brighter?
  - B. Why?
  - C. When in parallel, which light bulb is brighter?
  - D. Why?
  - E. Is your house in parallel or series?
  - F. Which is the bigger resistor: a 40W bulb or a 80W bulb?
6. The following questions will be easy if you work the circuit first.
  - A. What is the current flowing thru the  $3\Omega$  resistor?
  - B. How much voltage is used by the  $9\Omega$  resistor?
  - C. What is the voltage at point E?
  - D. How much power is used by the  $6\Omega$  resistor?
  - E. What is the total power used by the circuit?




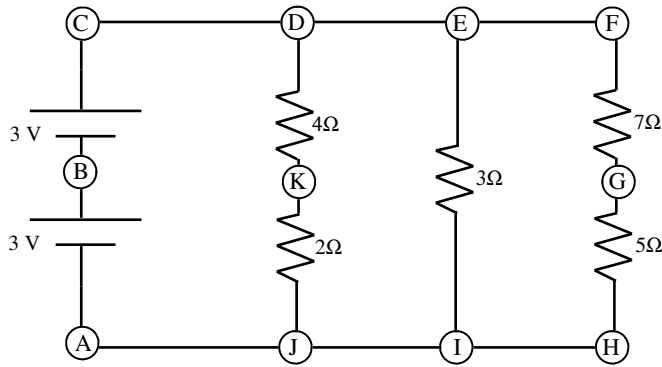


7. After you have worked the circuit, answer the following questions.
- What is the voltage at F?
  - What is the voltage at H?
  - What is the current from F to H?
  - What is the current from I to J?
  - What is the current from C to D?
  - What is the current in the 4Ω resistor?
  - What is the voltage used by the 4Ω resistor?
  - What is the voltage at point K?
  - What is the power used by the 3Ω resistor?
  - What is the total power used by the circuit?
  - Since  $P = W/t$  (or  $P = \text{Energy}/\text{time}$ ), how much energy is used by the whole circuit in 10 seconds?

8. Remembering that 1 electron =  $-1.6 \times 10^{-19} \text{C}$ ...
- How many electrons does it take to make a charge of  $6.8 \mu\text{C}$ ?

B. What is the charge of 8.5 electrons?

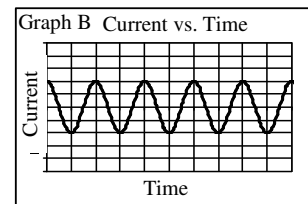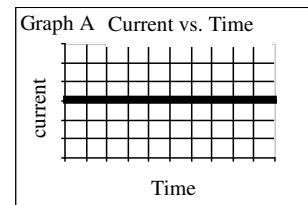9. AC current means “Alternating Current”. DC means “Direct Current”.
- Which graph at the right show AC?
  - Which graph shows DC?
  - Look at any device that plugs into a wall socket and figure out if your house uses AC or DC.
  - Look at a battery. Is it AC or DC?



10. An object has a charge of  $5.6 \mu\text{C}$ .
- Is it positive or negative?
  - Did it gain or lose electrons to have this charge?
  - If a  $-2 \mu\text{C}$  charge is brought near it, will they attract or repel each other?
  - As they are brought closer to each other, does the potential energy between them increase or decrease? (*Think of it like a spring.*)