
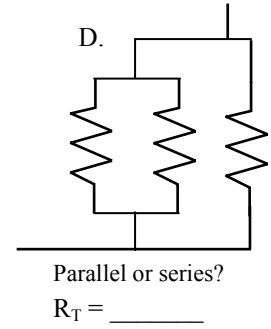
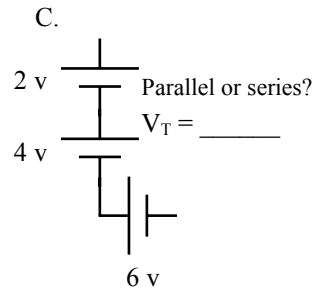
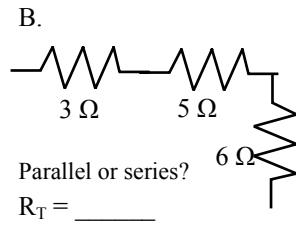


PreAP: Due: Wed., Jan 18 (Assigned: Fri., Jan 13)
 Reg: Due: Thurs., Jan 19 (Assigned: Tues., Jan 17)

Electricity 5

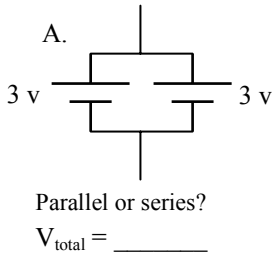1. Identify the following as parallel or series and find the total resistance or voltage.




2. If you connected A and B above, what would be the total current in the circuit?

3. If you connected C and D above, what would be the total current in the circuit?

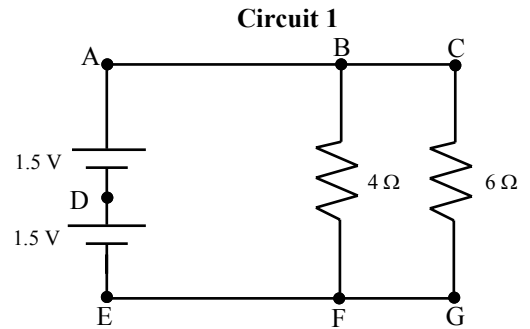4. Using Circuit 1, answer the following:

- $V_T = \underline{\hspace{2cm}}$
- Are the batteries in series or parallel?
- Are the resistors in series or parallel?
- Calculate the total resistance.



E. Find the total current in the circuit.




F. What are the following voltages? $V_{ED} = \underline{\hspace{2cm}}$; $V_{DA} = \underline{\hspace{2cm}}$; $V_{AB} = \underline{\hspace{2cm}}$; $V_{AE} = \underline{\hspace{2cm}}$;
 $V_{AG} = \underline{\hspace{2cm}}$; $V_{CG} = \underline{\hspace{2cm}}$;

G. Since you know the voltage across the 4 Ω resistor, find the current running through it.




H. Likewise, find the current through the 6 Ω resistor.

I. How does the voltage in each of the resistors compare with the total current in the circuit.

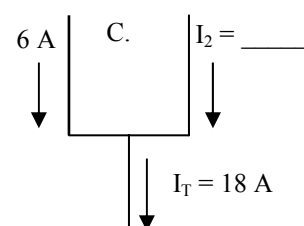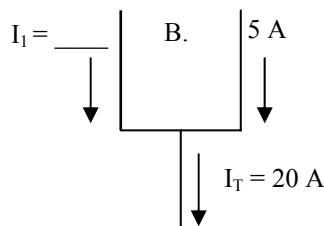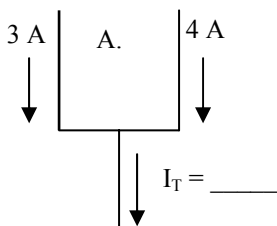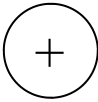5. Understanding junctions. Fill in the missing information on the following graphics:



6. Show the electric field lines for the following:

<p>A.</p> <div style="text-align: center; margin-top: 50px;">  </div>	<p>B.</p> <div style="text-align: center; margin-top: 50px;">  </div>	<p>C.</p> <div style="text-align: center; margin-top: 50px;">  </div>
--	--	--

7. If a circuit has 3 A of current, how much charge moves in 10 seconds?

8. Using your answer from #7, how many electrons moved in that 10 seconds?

9. Acids, bases and ionic compounds all _____ in water, creating s_____ that have ions. These ions are neutral or charged? Thus they will do what for electricity?

10. (From the 2004 Exit Level TAKS test): *The seawater in the setup at the right allows electricity to flow (meaning it is a _____) because it is a:*

- A. strong electrolyte
- B. weak acid
- C. nonelectrolyte
- D. strong base

11. The lightbulb is the _____ for this circuit.

12. The voltage generator is a _____.

