

Matching Circuit

Name: _____



1



2



3



4



5



6



7



8



A



B



C



D



E



F



G



H

