Name: \_\_\_

## Period:

## HW Unit 9:5—Voltage, Current, Resistance Mr. Murray, IPC cstephenmurray.com

## A-day: Due Wed., 3/28 (Assig: 3/26) B-day: Due Thurs., 3/29 (Assig: 3/27)

1. Resistance is measured in what units?

\_\_\_\_\_

- 2. Current is measured in what units?
- Voltage is measured in what units? 3.
- Which has more current a big river or small stream? 4.
- Which uses more current, a bright or dim light? 5.
- Which uses more current, a loud or soft radio? 6.
- 7. Which gives more voltage a big or small water pump?
- Which gives more voltage a 1.5V or 9V battery? 8.
- Which is has more voltage, water coming from the top of a 9. mountain or coming from the top of a table?
- 10. Which will have *less* resistance: an insulator or a conductor?
- 11. Which is a better *conductor*:  $200 \Omega$  or  $10 \Omega$ .

- 12. From my water demo.
  - A. Which hose had the most resistance: the big or small hose?
  - B. Which hose had the most current flowing: big or small?
  - C. When I lifted up the bucket, did the water flow more or less?
  - D. When I lifted the bucket, it was an example of more voltage, more current, or more resistance?
- 13. Find the total voltage of the following:



- 14. Do batteries use or create voltage?
- HW Unit 9:5

- 15. Do resistors use or create voltage?
- 16. A 24 V battery pushes thru a 6  $\Omega$  resistor. Find the current. Variables Equation Solve
- 17. If 6 A are flowing thru a 8  $\Omega$  resistor. Find the voltage. Variables Equation Solve
- 18. Mark where this circuit has high, medium, and low voltage.



- 19. Control, Experimental, or Responsive Variable?
  - A. \_\_\_\_ What you are studying in the experiment.
  - B. \_\_\_\_ There are many of these in a good experiment.
  - C. \_\_\_\_ What happens in the experiment.
  - D. \_\_\_\_ Only one of these in a good experiment.
- 20. When we were studying how voltage affected current:
  - A. Give two control variables.
  - B. What was our experimental variable?
  - C. What was our responsive variable?
- 21. When we were studying resistance:
  - A. What was our responsive variable?
  - B. What was our control variables?
  - C. What was our experimental variable?

Get your conclusion statements in.